Hardware Setup:

I started with the basic breadboard setup that was covered in class

IR Receiver:


The remote control that is used in this project is connected to the IR Receiver. The IR Receiver receives commands from the remote, which allow the player to move across the screen.


- Left Leg: GPIO 15
- Middle Leg: Ground/ Negative Rail
- Right Leg: Power/ Positive Rail


SPI OLED Display:

Pin Name	Color of Wire	Left Leg (Wire)	Right Leg (Wire)
CS	Yellow	e31	GPIO 20
RST	Blue	e30	GPIO 17
D/C	Purple	e29	GPIO 16
CLK	Green	e28	GPIO 18
DATA	Orange	e27	GPIO 19
VIN	White	e26	Power/Positive Rail
GND	Purple	e24	Ground/Negative Rail

Images:

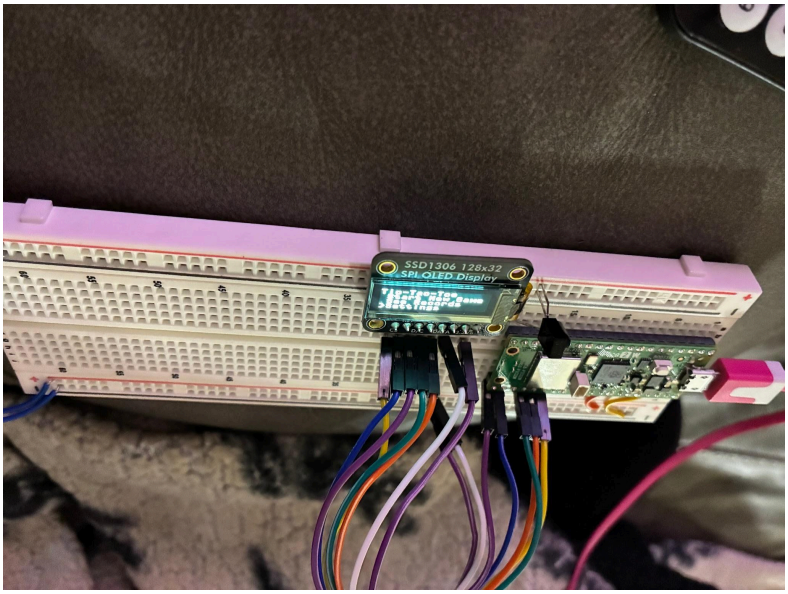
SSD1306 128x32
SPI OLED Display

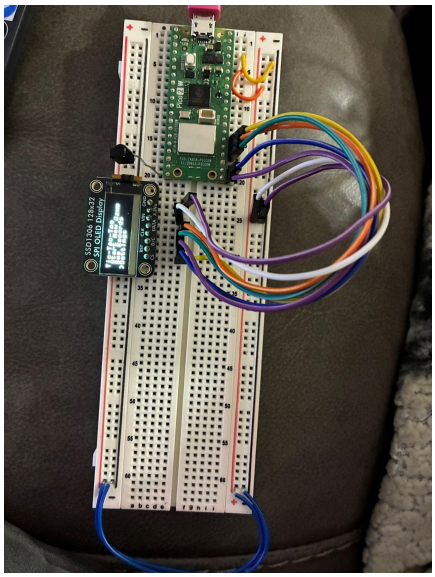

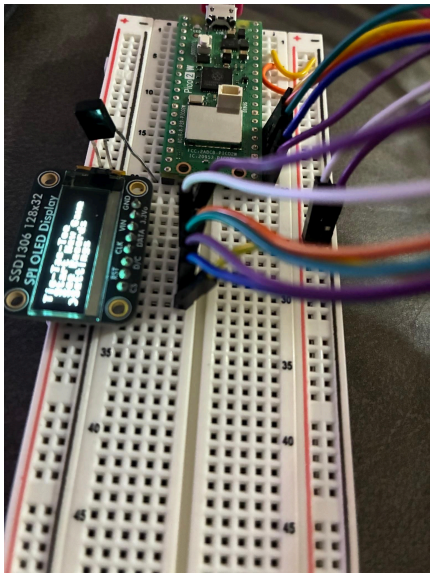
SSD1306 128x32
SPI OLED Display

